

The three boolean expression of  $G_3$ ,  $G_2$ ,  $G_1$  are realized using gates.

 


Fig. 3.51. Binary to gray code converter logic diagram

The logic diagram can be verified manually by putting the values of  $B_3$ ,  $B_2$  and  $B_1$  in the gates. If  $B_3$ ,  $B_2$  and  $B_1$  is 000 then  $G_3 = 0$  and  $G_2$  is obtained by taking EX-OR operation of  $B_2$  and  $B_3$ , which is again '0'. It means that  $G_2 = 0$ . The value of  $G_1$  is obtained by taking the EX-OR operation of  $B_1$  and  $B_2$  which produces '0' result. So  $G_1$  is zero. The values of  $G_3$   $G_2$   $G_1 = 000$  corresponding to  $B_3$   $B_2$   $B_1 = 000$  matched with the truth table. Hence, the logic diagram is verified.

### 3.18 PRIORITY ENCODER

When feeding data/program into a computer it is possible that more than one key is pressed simultaneously. A priority function means that the encoder will give priority to the highest order decimal digit in the inputs and ignore all other e.g. in a priority encoder decimals 8 and 4 are pressed together (i.e. both 8 and 4 inputs are high), the encoder will convert the decimal 8 to the output and ignore 4.

#### Decimal to BCD Priority Encoder

The logic circuit for incorporating a priority in encoding must incorporate a feature to prevent a lower order digit input from disrupting the encoding of higher order digit. This is done by using inhibit (enable) gates.

The truth table for decimal to BCD is given as :

Decimal Number	BCD Codes			
	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1

It is seen from the truth table that  $Y_0$  is high when inputs 1, 3, 5, 7, 9 are high. Priority can be added if digit 1 input activates gates  $Y_0$  only if no higher digit (other than which also activate  $Y_0$ ) are high. This is expressed as :

- (1)  $Y_0$  is high if 1 is high and 2, 4, 6, 8 are low
- (2)  $Y_0$  is high if 3 is high and 4, 6, 8 are low
- (3)  $Y_0$  is high if 5 is high and 6, 8 are low
- (4)  $Y_0$  is high if 7 is high and 8 is low
- (5)  $Y_0$  is high if 9 is high.

The 5 statements describe the priority for encoding for BCD bit  $Y_0$ . Thus  $Y_0$  is high if any of above statements are true.

The logic equation is expressed as :

$$Y_0 = 1 \cdot \bar{2} \cdot \bar{4} \cdot \bar{6} \cdot \bar{8} + 3 \cdot \bar{4} \cdot \bar{6} \cdot \bar{8} + 5 \cdot \bar{6} \cdot \bar{8} + 7 \cdot \bar{8} + 9$$

The logic statement for  $Y_1$  is given as :

2,3,6,7

- (1)  $Y_1$  is high if 2 is high and 4, 5, 8, 9 are low.
- (2)  $Y_1$  is high if 3 is high and 4, 5, 8, 9 are low.
- (3)  $Y_1$  is high if 6 is high and 8, 9 are low
- (4)  $Y_1$  is high if 7 is high and 8, 9 are low

The above statements can be expressed as

$$Y_1 = 2 \cdot \bar{4} \cdot \bar{5} \cdot \bar{8} \cdot \bar{9} + 3 \cdot \bar{4} \cdot \bar{5} \cdot \bar{8} \cdot \bar{9} + 6 \cdot \bar{8} \cdot \bar{9} + 7 \cdot \bar{8} \cdot \bar{9}$$

The output  $Y_2$  can be described by following statements :

4567

- (1)  $Y_2$  is high if 4 is high and 8, 9 are low
- (2)  $Y_2$  is high if 5 is high and 8, 9 are low
- (3)  $Y_2$  is high if 6 is high and 8, 9 are low
- (4)  $Y_2$  is high if 7 is high and 8, 9 are low.

It is expressed as logic equation

$$Y_2 = 4 \cdot \bar{8} \cdot \bar{9} + 5 \cdot \bar{8} \cdot \bar{9} + 6 \cdot \bar{8} \cdot \bar{9} + 7 \cdot \bar{8} \cdot \bar{9}$$

The statement for  $Y_3$  is given as :

89

- (1)  $Y_3$  is high if 8 is high and 9 is low.
- (2)  $Y_3$  is high if 9 is high.

Logical equation is given as for  $Y_3$  i.e.

$$Y_3 = 8 \cdot \bar{9} + 9 \quad 8 + 9 \quad [\because A\bar{B} + B = A + B]$$



Truth table realization is given as :

Inputs										Output			
9	8	7	6	5	4	3	2	1	0	$Y_3$	$Y_2$	$Y_1$	$Y_0$
0	0	0	0	0	0	0	0	0	1	0	0	0	0
0	0	0	0	0	0	0	0	1	x	0	0	0	1
0	0	0	0	0	0	0	1	x	x	0	0	1	0
0	0	0	0	0	0	1	x	x	x	0	0	1	1
0	0	0	0	0	1	x	x	x	x	0	1	0	0
0	0	0	0	1	x	x	x	x	x	0	1	0	1
0	0	0	1	x	x	x	x	x	x	0	1	1	0
0	0	1	x	x	x	x	x	x	x	0	1	1	1
0	1	x	x	x	x	x	x	x	x	1	0	0	0
1	x	x	x	x	x	x	x	x	x	1	0	0	1

Logic circuit for output bit  $Y_0, Y_1, Y_2, Y_3$  is given as follows :

 


Fig. 3.52. Logic circuit for output bit  $Y_0$  of decimal to BCD Priority encoder.

 
 
 


Fig. 3.53. Logic circuit for output bit  $Y_1$ .


 Fig. 3.54. Logic circuit for output bit  $Y_2$ .

 Fig. 3.55. Logic circuit output of  $Y_3$ .

### 3.19 DECODER

A decoder is a combinational circuit that converts an  $N$ -bit binary input code into  $M$  output lines such that only one output line is activated for each one of the possible combinations of inputs. The block diagram for decoder is shown as in figure 3.56.

 


Fig. 3.56.

Since each of  $N$  inputs can be 0 or 1, there are  $2^N$  possible input combinations or codes. For each of these input combinations, only one of  $M$  outputs will be active (High), all the other outputs will remain inactive (Low). Some decoders are designed to produce active low output, while all the other outputs remain



high. Some decoders do not utilize  $2^N$  possible input codes e.g. a BCD to decimal decoder.

Examples of decoders are :

### (1) 3 Line to 8 Line Decoder

For this decoder, it has three inputs and 8 outputs. It uses all AND gates, therefore the outputs are active high. For active low outputs NAND gates are used. This decoder is also known as binary to octal decoder. The truth table is given as :

Inputs			Outputs							
A	B	C	$D_0$	$D_1$	$D_2$	$D_3$	$D_4$	$D_5$	$D_6$	$D_7$
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

The logic diagram is represented as follows :

 


Fig. 3.57.

## (2) BCD to Decimal Decoder

4:10

In this decoder BCD is input and decimal number is output. It is also known as 4 to 10 line decoder. The truth table is given as follows :

Input BCD Code				Actual Output	
$A_3$	$A_2$	$A_1$	$A_0$		
0	0	0	0	_____	$\overline{D_0}$
0	0	0	1	_____	$\overline{D_1}$
0	0	1	0	_____	$\overline{D_2}$
0	0	1	1	_____	$\overline{D_3}$
0	1	0	0	_____	$\overline{D_4}$
0	1	0	1	_____	$\overline{D_5}$
0	1	1	0	_____	$\overline{D_6}$
0	1	1	1	_____	$\overline{D_7}$
1	0	0	0	_____	$\overline{D_8}$
1	0	0	1	_____	$\overline{D_9}$

For input combinations that are invalid for BCD, none of the outputs will be activated. In this case, we assume the output should be active low, for this we use NAND gates instead of AND gate. The circuit representation is given as follows :

 


Fig. 3.58. 4 Line to 10 line decoder.

### (3) Binary to Gray Code converter

The conversion table for binary to Gray Code is given as follows :



Decimal No.	Binary				Gray			
	$B_1$	$B_2$	$B_3$	$B_4$	$G_1$	$G_2$	$G_3$	$G_4$
0	0	0	0	0	0	0	0	0
1	0	0	0	1	0	0	0	1
2	0	0	1	0	0	0	1	1
3	0	0	1	1	0	0	1	0
4	0	1	0	0	0	1	1	0
5	0	1	0	1	0	1	1	1
6	0	1	1	0	0	1	0	1
7	0	1	1	1	0	1	0	0
8	1	0	0	0	1	1	0	0
9	1	0	0	1	1	1	0	1
10	1	0	1	0	1	1	1	1
11	1	0	1	1	1	1	1	0
12	1	1	0	0	1	0	1	0
13	1	1	0	1	1	0	1	1
14	1	1	1	0	1	0	0	1
15	1	1	1	1	1	0	0	0

The K-map realization for  $G_1$ ,  $G_2$ ,  $G_3$  and  $G_4$  is given as follows :

$B_3 B_4$ \ $B_1 B_2$	00	01	11	10
00	0	0	1	1
01	0	0	1	1
11	0	0	1	1
10	0	0	1	1

$$G_1 = B_1$$

$B_3 B_4$ \ $B_1 B_2$	00	01	11	10
00	0	1	0	1
01	0	1	0	1
11	0	1	0	1
10	0	1	0	1

$$G_2 = \overline{B_1} B_2 + B_2 \overline{B_1} = B_1 \oplus B_2$$

$B_3 B_4$ \ $B_1 B_2$	00	01	11	10
00	0	1	1	0
01	0	1	1	0
11	1	0	0	1
10	1	0	0	1

$$G_3 = \overline{B_2} B_3 + B_2 \overline{B_3} = B_2 \oplus B_3$$

$B_3 B_4$ \ $B_1 B_2$	00	01	11	10
00	0	0	0	0
01	1	1	1	1
11	0	0	0	0
10	1	1	1	1

$$G_4 = \overline{B_3} B_4 + B_3 \overline{B_4} = B_3 \oplus B_4$$

The circuit realization of binary to Gray Code converter is given as :