

Fig. 3.59. Circuit Diagram for Binary to Gray Code Decoder

3.20 MAGNITUDE COMPARATOR

Magnitude comparator is one of the useful combinational logic networks and has wide application. [It compares two binary numbers and determines one number is greater than, less than or equal to the other number.] It is a multiple output combinational logic circuit. If two binary numbers are considered as A and B , the magnitude comparator gives three output for $A > B$, $A < B$ and $A = B$.

The comparator will do the comparison from the most significant bit (i.e. A_3 and B_3), then result is $A > B$. If the MSB's are equal, then next bit i.e. A_2 and B_2 is compared and so on until the least significant bit is reached.

1-Bit Comparator Circuit

For 1-bit circuit only two bits are there i.e. $0 < 1$. The truth table for 1-bit is given as follows :

Inputs		Outputs		
A	B	$A > B$	$A = B$	$A < B$
0	0	0	1	0
1	0	1	0	0
0	1	0	0	1
1	1	0	1	0

For Bit $A = 0$ and $B = 0$, the output is $A = B$, hence output corresponding to $A = B$ is high and rest two outputs $A > B$ and $A < B$ is low. Similarly for $A = 1$ and $B = 1$, output $A = B$ is high and for $A = 1$ and $B = 0$, output $A > B$ is high and for last combination i.e. $A = 0 < B = 1$, $A < B$ output bit is high.

Designing of 1-bit Comparator

For

$$A > B$$

Output expression is given as $\Rightarrow A \bar{B}$

For

$$A = B$$

$$\text{Output} = \bar{A} \bar{B} + AB$$

For

$$A < B$$

$$\text{Output} = \bar{A} B$$

 


Fig. 3.60. Designing of 1-bit Comparator.

2-Bit Comparator

For 2-bit comparator the truth table is given as follows :

Let us represent the input A by two bits i.e. $A_0 A_1$ and input B by $B_0 B_1$. The outputs are $A > B$, $A < B$ and $A = B$. The outputs are obtained by comparing the bits A_0, B_0, A_1, B_1 .

The truth table is as follows :

Inputs				Outputs		
A_0	A_1	B_0	B_1	$A > B$	$A = B$	$A < B$
0	0	0	0	0	1	0
0	0	0	1	0	0	1
0	0	1	0	0	0	1
0	0	1	1	0	0	1
0	1	0	0	1	0	0
0	1	0	1	0	1	0
0	1	1	0	0	0	1
0	1	1	1	0	1	0
1	0	0	0	1	0	0
1	0	0	1	1	0	0
1	0	1	0	0	1	0
1	0	1	1	0	0	1
1	1	0	0	1	0	0
1	1	0	1	1	0	0
1	1	1	0	1	0	0
1	1	1	1	0	1	0

The K-map realization for $A > B$, $A = B$ and $A < B$ is given as follows :

$A_0 A_1$	00	01	11	10
$B_0 B_1$	00	0	1	1
	01	0	1	1
	11	0	0	0
	10	0	1	0

$A_0 A_1$	00	01	11	10
$B_0 B_1$	00	0	0	0
	01	0	1	0
	11	0	0	1
	10	0	0	1

$$A > B = A_0 \bar{B}_0 + A_1 \bar{B}_0 \bar{B}_1 + \bar{B}_1 A_0 A_1$$

$$A = B \Rightarrow \bar{A}_0 \bar{A}_1 \bar{B}_0 \bar{B}_1 + \bar{A}_0 A_1 \bar{B}_0 B_1 + A_0 A_1 B_0 B_1 + A_0 \bar{A}_1 B_0 \bar{B}_1$$

$A_0 A_1$	00	01	11	10
$B_0 B_1$	00	0	0	0
	01	1	0	0
	11	1	1	0
	10	1	1	0

$$A > B = \bar{A}_0 B_0 + \bar{A}_0 \bar{A}_1 \bar{B}_1 + \bar{A}_1 B_0 B_1$$

Circuit Designing is shown in figure 3.61, 3.62 and 3.63.

 


Fig. 3.61.

 


Fig. 3.62.

 


Fig. 3.63.

EXAMPLE 3.11. Implement the function $F(A, B, C) = \Sigma(1, 3, 5, 6)$ using decoder.

Solution: Since the function has 3-inputs variables, a 3 to 8 line decoder may be used. It is in the sum of the products of minterms m_1, m_3, m_5 and m_6 and so decoder output D_1, D_3, D_5 and D_6 may be OR gated to achieve the desired function. The designing is as follows :

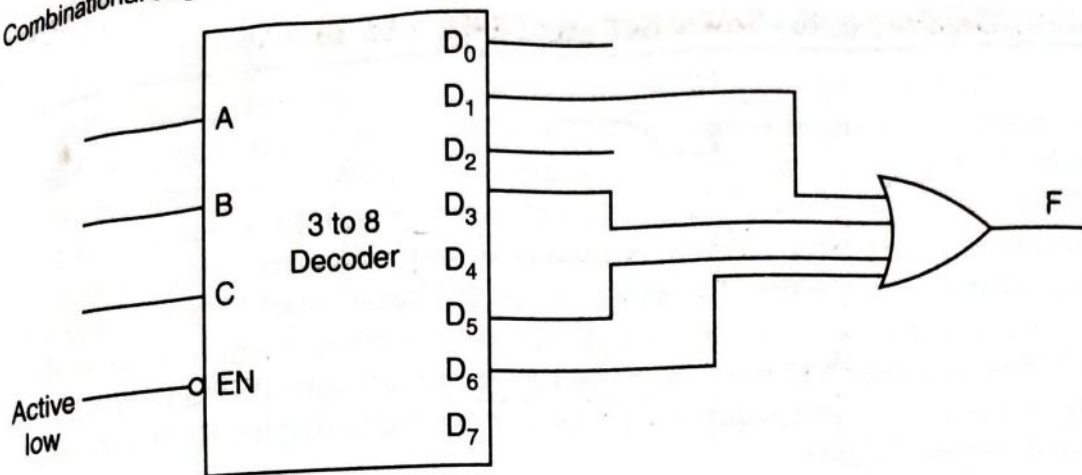


Fig. 3.64.

EXAMPLE 3.12. Design a full adder with decoder.

Solution: The output expression for sum and carry is given as :

$$S = \bar{X}\bar{A}B + \bar{X}A\bar{B} + X\bar{A}\bar{B} + XAB \quad \begin{matrix} 001 + 010 + 100 + 111 \\ 1 \quad 2 \quad 4 \quad 7 \end{matrix}$$

$$C = \bar{X}AB + X\bar{A}B + XA\bar{B} + XAB \quad \begin{matrix} 011 + 101 + 110 + 111 \\ 3 \quad 5 \quad 6 \quad 7 \end{matrix}$$

The designing is as follows :

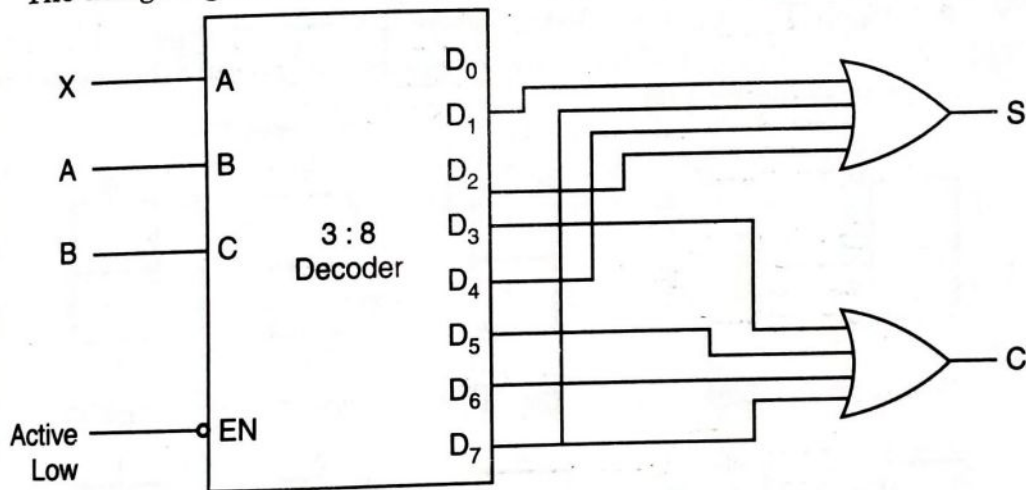


Fig. 3.65.

EXAMPLE 3.13. Design full subtractor using decoder.

Solution: The output expression for borrow and difference is as follows :

$$D = \bar{X}\bar{Y}Z + \bar{X}Y\bar{Z} + X\bar{Y}\bar{Z} + XYZ \quad \begin{matrix} 001 \quad 010 \quad 100 \quad 111 \\ 1 \quad 2 \quad 4 \quad 7 \end{matrix}$$

$$B = \bar{X}\bar{Y}Z + \bar{X}Y\bar{Z} + \bar{X}YZ + XYZ$$

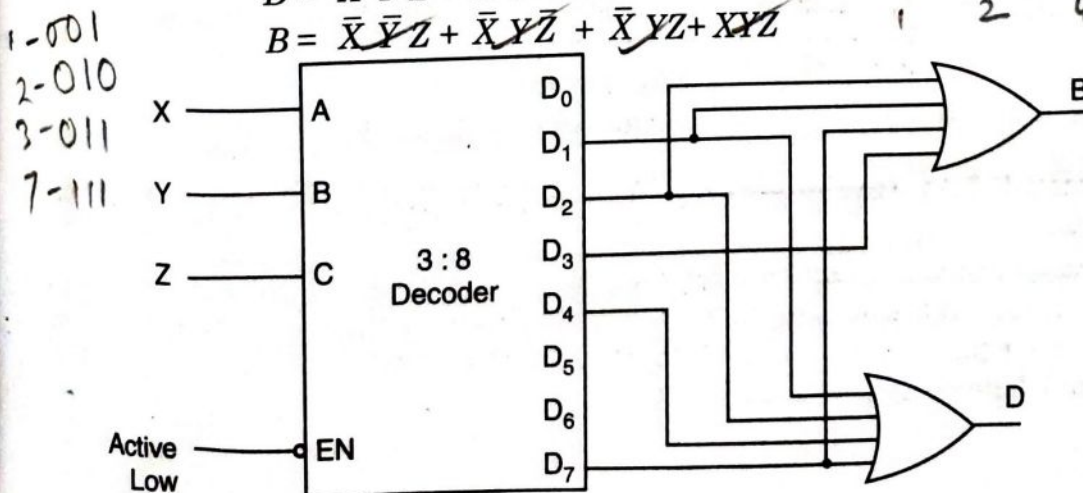


Fig. 3.66.