

$$\Delta t = \frac{n}{f}$$

where  $f$  = clock frequency in MHz

$n$  = number of stages

$\Delta t$  = time delay in  $\mu s$

e.g. 4-bit register having clock frequency of 2 MHz, calculate the time delay

The time delay is given as

$$\Delta t = \frac{n}{f} = \frac{4}{2}$$

$$\Delta t = 2\mu s$$

### 4.31 COUNTER

Counter is special sequential device which is used to count the clock pulses.

A counter have number of binary state which progress in defined fixed sequential manner.

Or

A counter is an sequential machine that is constructed with the help of flip-flop and it changes its state according to the state diagram.

Or

A counter is basically a register that is capable of counting the number of clock pulses that are available at its clock input.

The counting of counter may be ascending, descending or in any manner defined by the designer.

#### For example:

A single J-K flip-flop can acts as an counter which counts two states as shown in below diagram.

When positive edge of clock is arrived then the J-K flip-flop changes its state from 0 to 1 or 1 to 0.

Let us assume initially the flip-flop is in reset condition i.e.,  $Q_{n+1} = 0$  and we apply the input  $J = K = 1$  hence the output is given as

$$Q_{n+1} = \bar{Q}_n$$

where  $Q_{n+1}$  = Next state  
 $Q_n$  = Present state

 


Fig. 4.128.

Clock

$$Q_{n+1} = Q_n$$

State D



F

State

Arrow

changed

Count

(i) M

(ii) M

(iii) M

(iv) M

### 4.31.1

Cou

is equi

Accord

(i)

as sho

Fig


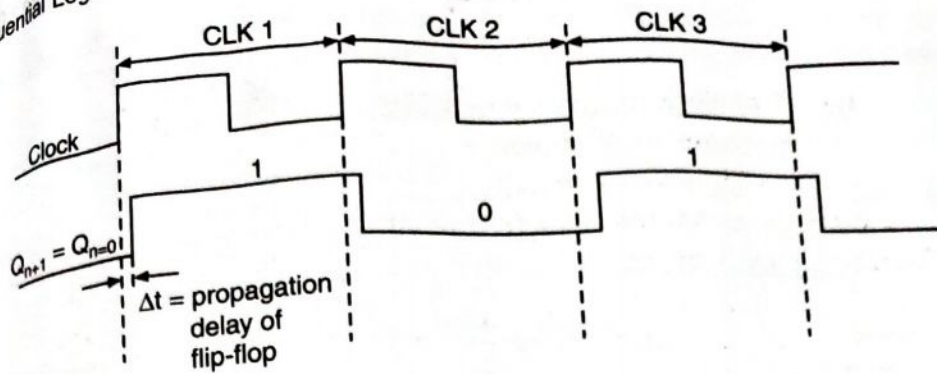


Fig. 4.129. Waveform of 1 bit counter

State Diagram: For single bit counter

 

Truth Table

Clock	Output ( $Q_{n+1}$ )
↑	1
↑	0
↑	1

repeating sequence

FIG. 4.130.

State diagram consist of circle which contains the binary value.

Arrows in state diagram show the progress sequence of the counter. State is changed on arrival of clock pulse. For each clock pulse one state is changed.

Counter can be classified on the basis of following factors.

- (i) Number of output bits or Number of flip-flop.
- (ii) Number of states or modulus counter.
- (iii) Single mode and multimode counter.
- (iv) Synchronous and Asynchronous counter.

#### 4.31.1. Number of Output Bits or Number of Flip-Flop

Counters can be classified on the basis of flip-flop used. One flip-flop output is equivalent to one bit of the counter. So, it is also known as binary counters. According to this criteria the flip-flop are

(i) **Single bit Binary Counter:** Single bit counter consist of two state 0, 1 as shown below in state diagram.

 


Fig. 4.131. State diagram of 1 bit counter

 


Fig. 4.132.



For single bit counter the input of  $T$  is high and the state is changed when positive edge of clock is arrived. Initially output is considered as '0'.

 


Fig. 4.133.

## Truth Table

Clock	Output ( $Q_{n+1}$ )
↑	1
↑	0
↑	1

repeating sequence

(ii) **2-bit Counter:** As the name suggested two bit counter consist of two flip-flop arranged in given below manner.

 


Fig. 4.134. 2-bit Ripple/Asynchronous Counter

2-bit counter shown (Ripple) in above figure is an **asynchronous counter** in which all flip-flop are not Synchronized (means clock is not common to all flip flops).

Preset and clear inputs are used to set the output of counter i.e., initialization to "00" or to "11" output. The input  $T$  of the flip-flop is always connected to high logic (means '1').

## State Diagram

 


Fig. 4.135.

The four possible state of the 2 bit counter is shown in figure.

Truth Table

Clock pulse	Output	
	$Q_1$ (MSB)	$Q_0$ (LSB)
1.	0	0
2.	0	1
3.	1	0
4.	1	1
5.	0	0

→ repetition/  
recycle

From the above truth table it is cleared that 2 bit counter can counts four value and the functionality can be better understandable using waveform.

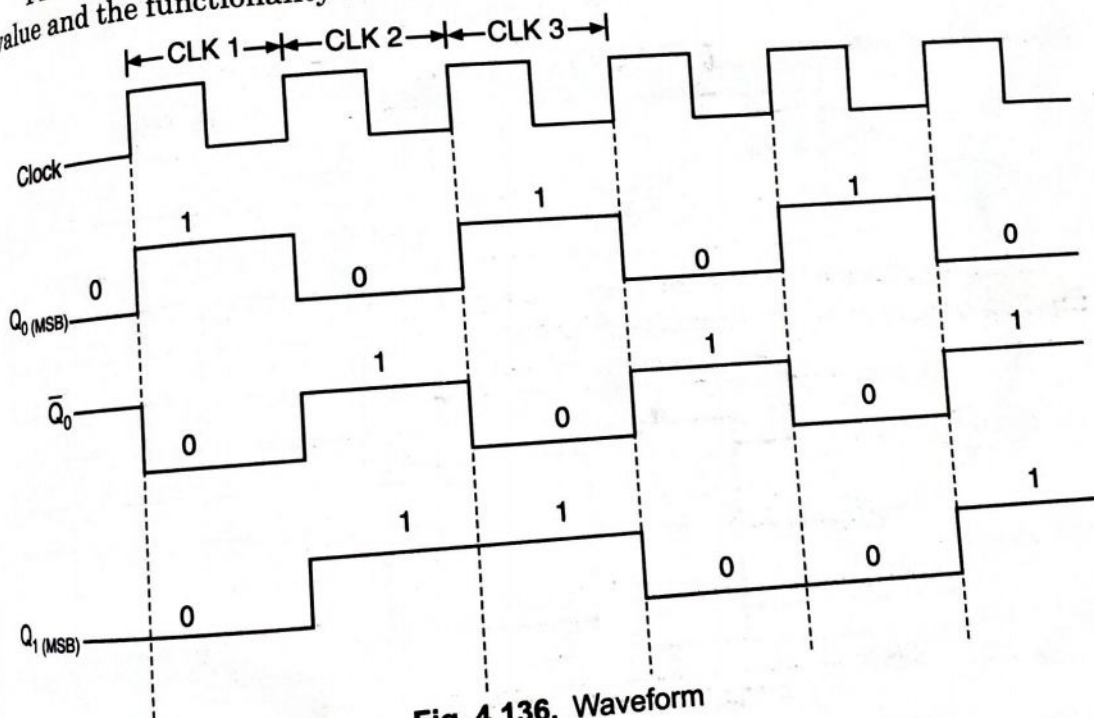


Fig. 4.136. Waveform

### Working

The working of 2 bit Asynchronous counter can be easily understandable if we have knowledge about the working of T-flip-flop.

When input  $T = 1$  then output  $Q_{n+1} = \bar{Q}_n$  i.e., Toggle hence on arrival of positive edge of clock pulse the output is just opposite of previous output.

The output  $\bar{Q}_0$  is feeded to the clock input of flip-flop 1 hence when positive edge of  $\bar{Q}_0$  is arrived then FF1 changes its state which can be better understandable from waveform figure.

(iii) **3-bit Counter:** 3 bit counter consist of 3 flip-flop as shown in below figure.




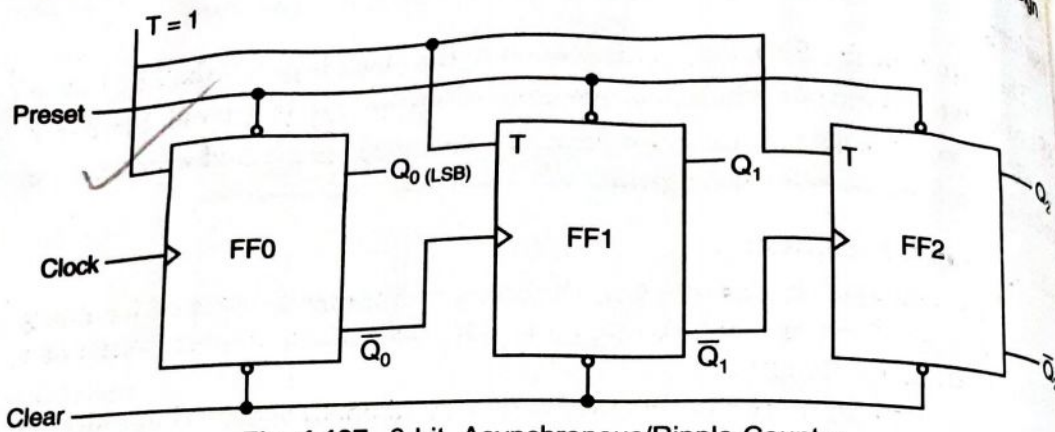


Fig. 4.137. 3-bit Asynchronous/Ripple Counter

Clock pulse is applied to FF0 and the output,  $\bar{Q}_0$  of the FF0 is feeded to clock of FF-1 and similarly the output,  $\bar{Q}_1$  of the FF-1 is feeded to clock of FF-2.

#### State Diagram

 

Truth Table

$Q_2$ (MSB)	$Q_1$	$Q_0$ (LSB)
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

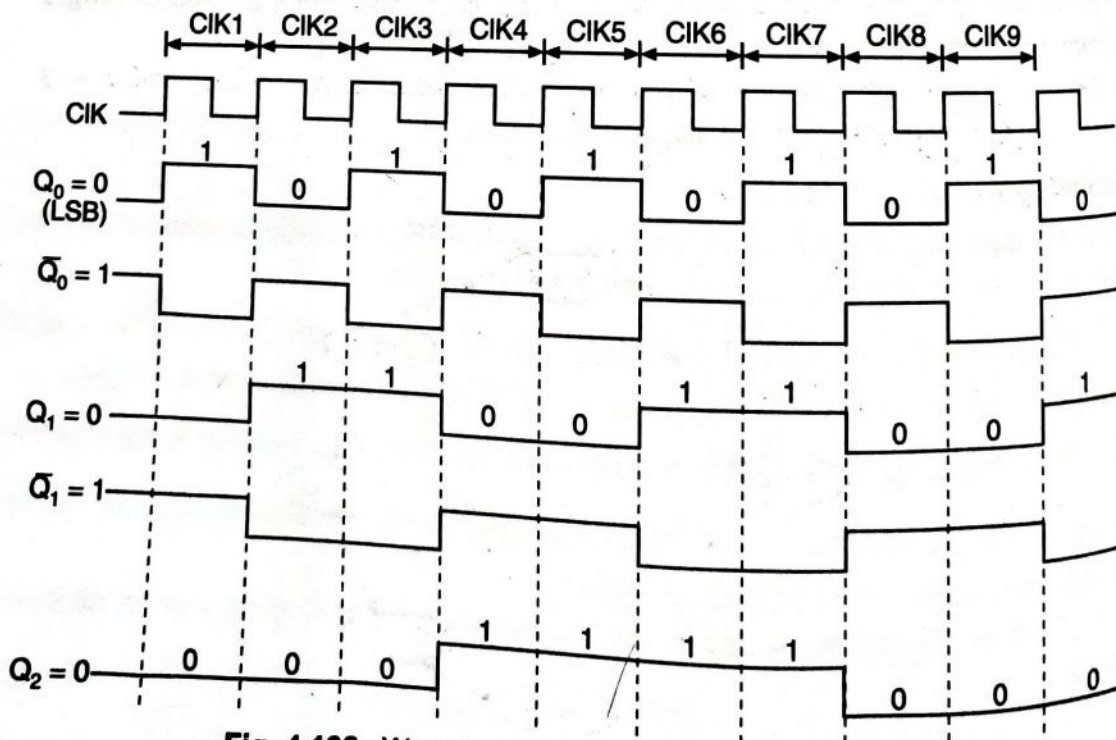


Fig. 4.138. Waveform of 3 bit asynchronous counter

Sequential Logic Circuit  
**Working**

The output of the FF1 calculate its output and the FF2 calculates its output and understand from working.

#### 4.31.2. Modulus Counter

A counter can be designed to count only a specific number of possible states in a sequence.

Modulus counter design modulus of an Synchronous counter denotes '5' states.

(i) **Modulus Counter**  
& 1) and only single state.

Hence modulus counter.

#### 4.31.3. Synchronous Counter

A counter can be designed in a synchronous manner i.e., all flip-flops are clocked together.

For example, a 4-bit synchronous counter will recycle again after 16 states.

#### Designing a Counter

(i) State Diagram

**Working**

The output of the FF0, i.e.,  $\bar{Q}_0$  is feeded to the clock input of the FF1 hence FF1 calculate its output when positive edge of output  $\bar{Q}_0$  is arrived. Similarly the FF2 calculates its output when positive edge of  $\bar{Q}_1$  is arrived which can be understand from waveform diagram.

**4.31.2. Modulus Counter**

Counter can also be classified on the basis of number of states. Modulus-2 counter consist of two possible state, similarly modulus-4 counter consist of 4 possible states in an counter.

Modulus counter may be synchronous or asynchronous. Generally for design modulus counter designer uses synchronous technique because design of an Synchronous counter is easier than asynchronous counter. e.g., MOD-5 denotes '5' states i.e., from 0 to 4 (000, 001, 010, 011, 100).

(i) **Modulus-2 Counter:** Modulus-2 counter consist of only two state (i.e., 0 & 1) and only single flip-flop is enough to design mod-2 counter.

 


Fig. 4.139.

Hence mod-2 counter is similar to single bit counter.

**4.31.3. Single Mode and Multimode Counter**

A counter is said to be single mode if it counts the clock pulses in single manner i.e., ascending order or in descending order.

For example: UP counter which counts its value in ascending order and recycle agains from its initial value.

**Designing of up Counter:**

(i) State Diagram

 


Fig. 4.140.



By using state diagram we construct the state variable assignment table as shown below.

In up counter the counter counts in ascending order of decimal number i.e., 0, 1, 2, 3, 4...

← Filled using Excitation table

Present State			Next State			$D_2$ (MSB)	$D_1$	$D_0$ (LSB)
$Q_2$	$Q_1$	$Q_0$	$Q_2$	$Q_1$	$Q_0$			
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	0
0	1	0	0	1	1	0	1	1
0	1	1	1	0	0	1	0	0
1	0	0	1	0	1	1	0	1
1	0	1	1	1	0	1	1	0
1	1	0	1	1	1	1	1	1
1	1	1	0	0	0	0	0	0

The flip-flop is selected for construction of 3 bit up counter is D flip-flop.

Now use solve the equation of  $D_2$ ,  $D_1$ ,  $D_0$  with the help of k-map and implement using DFF.

$$D_2(Q_2, Q_1, Q_0) = \sum m(3, 4, 5, 6)$$

[for  $D_2$  the value is high at minterms 3, 4, 5 & 6]


$$D_1(Q_2, Q_1, Q_0) = \sum m(1, 2, 5, 6)$$

[for  $D_1$ , the value is high at minterms 1, 2, 5 & 6]

$$D_0(Q_2, Q_1, Q_0) = \sum m(0, 2, 4, 6)$$

[for  $D_0$ , the value is high at minterms 0, 2, 4, 6]


For  $D_2$

 

$$\begin{aligned}
 D_2 &= \bar{Q}_2 Q_1 Q_0 + Q_2 \bar{Q}_0 + Q_2 \bar{Q}_1 \\
 &= \bar{Q}_2 Q_1 Q_0 + Q_2 (\bar{Q}_0 + \bar{Q}_1)
 \end{aligned}$$

Sequential Logic Circuits and  
For  $D_1$

Implement the  
combinational circuit

 

Preset

Clock

Clear

Output

For  $D_1$

 


Fig. 4.142.

$$D_1 = Q_1 \bar{Q}_0 + \bar{Q}_1 Q_0$$

$$= Q_1 \oplus Q_0$$

 


Fig. 4.143.

$$D_0 = \bar{Q}_0$$

Implement the equation of  $D_2$ ,  $D_1$ ,  $D_0$  with help of Flip-Flop and combinational circuits as.

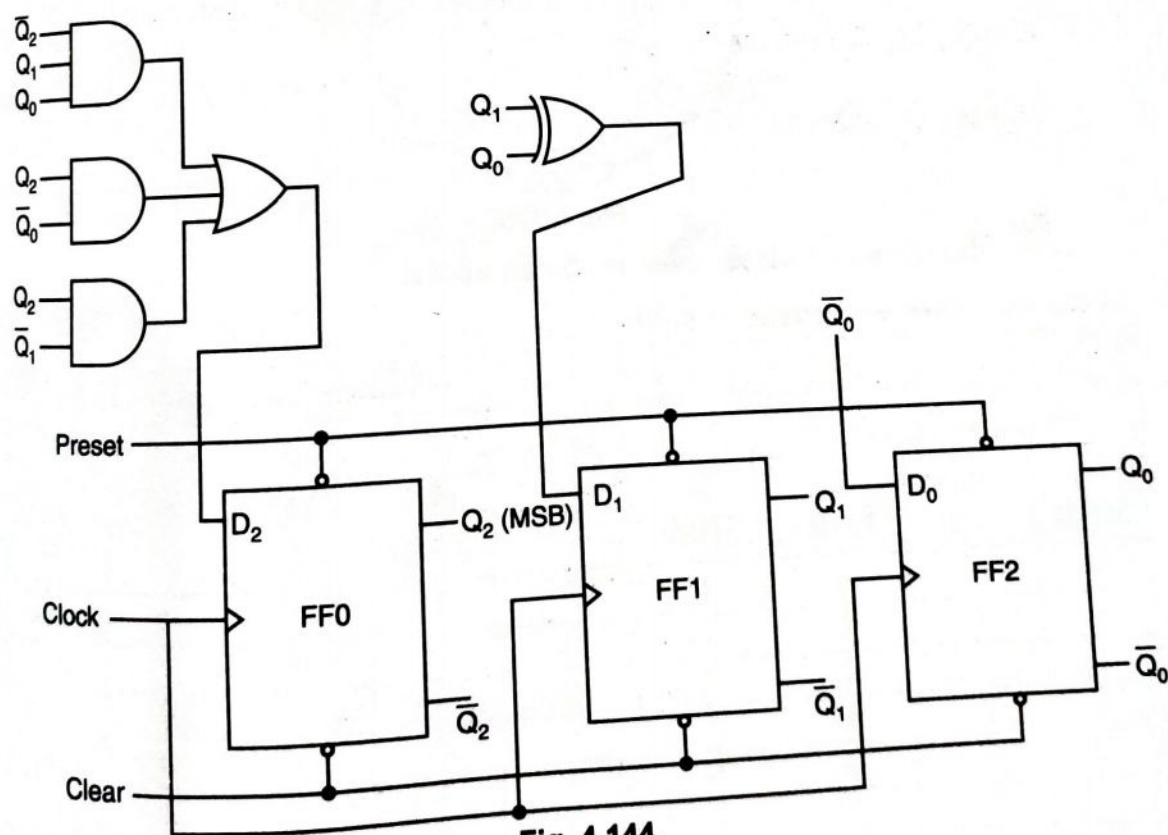


Fig. 4.144.

Output of the 3 bit up-counter is taken from  $Q_2$  (MSB),  $Q_1$ ,  $Q_0$  (LSB).



**Note:** Excitation table for flip-flop is given as:

It is used for designing and determine the inputs from outputs ( $Q_n, Q_{n+1}$ ).

$Q_n$ (Present State)	$Q_{n+1}$ (Next State)	S Flip-Flop		R Flip-Flop		J Flip-Flop		K Flip-Flop		T Flip-Flop		D Flip-Flop	
0	0	0		x		0		x		0		0	
0	1	1		0		1		x		1		1	
1	0	0		1		x		1		1		0	
1	1	x		0		x		0		0		1	

**Down Counter:** Down counter is also an single mode counter which can counter its value in descending order only. Down counter works descending order of decimal number i.e., 7, 6, 5, 4, 3, 2, 1, 0, 7, 6...

For designing the down counter first of all we make its state diagram and then state assignment table as shown below.

**State Diagram:**

 


Fig. 4.145.

State diagram of 3 bit counter is shown above.

**State variable assignment table**

←Using Excitation Table→								
Present State			Next State			$D_2$	$D_1$	$D_0$
$Q_2$ MSB	$Q_1$	$Q_0$ LSB	$Q_2$ MSB	$Q_1$	$Q_0$ LSB			
0	0	0	1	1	1	1	1	1
1	1	1	1	1	0	1	1	0
1	1	0	1	0	1	1	0	1
1	0	1	1	0	0	1	0	0
1	0	0	0	1	1	0	1	1
0	1	1	0	1	0	0	1	0
0	1	0	0	0	1	0	0	1
0	0	1	0	0	0	0	0	0

Sequential Logic Circuits  
Now solve the e

For  $D_2$

For  $D_1$

For  $D_0$

Now im  
combination

$D_0 = \bar{Q}_0$

Now implementing the equation of  $D_2, D_1, D_0$  using D Flip-Flop and combinational circuit.





In asynchronous counter the output of one flip-flop is feeded to clock input of other flip-flop which is shown in below diagram.

 


Fig. 4.151. 3-bit asynchronous counter (as different clock pulse is applied)

### 4.32 COMPARISON BETWEEN ASYNCHRONOUS AND SYNCHRONOUS COUNTER

- Asynchronous counter is a type of counter in which clock pulse is not common to all the flip-flops. For first flip-flop clock pulse is given and for other means 2<sup>nd</sup> flip-flop, the output of first flip-flop is acting as a clock to next flip-flop and so on while in Synchronous counter the clock pulse is common to all the flip-flops.
- Asynchronous counter (Ripple Counter) is also known as serial counter while Synchronous counter is known as parallel counter.
- Asynchronous counter (divide by N or Ripple Counter) is simpler to design while synchronous counter is difficult to design.
- Asynchronous counter requires the least amount of hardware as compared to Synchronous Counter.
- In asynchronous counter unwanted spikes are produced which is not present in Synchronous Counter.

#### Asynchronous Counter/Ripple Counter

In asynchronous counter, the output of one flip flop is feeded to clock input of other flip-flop as shown in fig. 4.155.

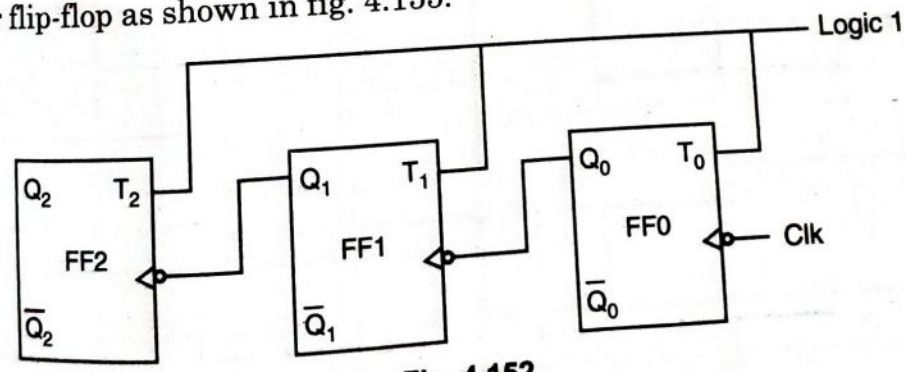


Fig. 4.152.

In this the Clk input drives FF0 and output of FF0 ( $Q_0$ ) drives FF1 and output of FF1 ( $Q_1$ ) drives FF2 which indicates a kind of asynchronous counter. T inputs i.e.,  $T_0, T_1, T_2$  are connected to logic 1. Here, each flip flop toggles at the negative edge of CLk pulse (as bubble is shown in clock pulse). As output of one flip flop (F/F) drives clock input of other, hence it is called as an asynchronous counter and as trigger moves like a ripple in water, hence it is



In asynchronous counter the output of one flip-flop is feeded to clock input of other flip-flop which is shown in below diagram.

 


Fig. 4.151. 3-bit asynchronous counter (as different clock pulse is applied)

#### 4.32 COMPARISON BETWEEN ASYNCHRONOUS AND SYNCHRONOUS COUNTER

- Asynchronous counter is a type of counter in which clock pulse is not common to all the flip-flops. For first flip-flop clock pulse is given and for other means 2<sup>nd</sup> flip-flop, the output of first flip-flop is acting as a clock to next flip-flop and so on while in Synchronous counter the clock pulse is common to all the flip-flops.
- Asynchronous counter (Ripple Counter) is also known as serial counter while Synchronous counter is known as parallel counter.
- Asynchronous counter (divide by N or Ripple Counter) is simpler to design while synchronous counter is difficult to design.
- Asynchronous counter requires the least amount of hardware as compared to Synchronous Counter.
- In asynchronous counter unwanted spikes are produced which is not present in Synchronous Counter.

#### Asynchronous Counter/Ripple Counter

In asynchronous counter, the output of one flip flop is feeded to clock input of other flip-flop as shown in fig. 4.155.

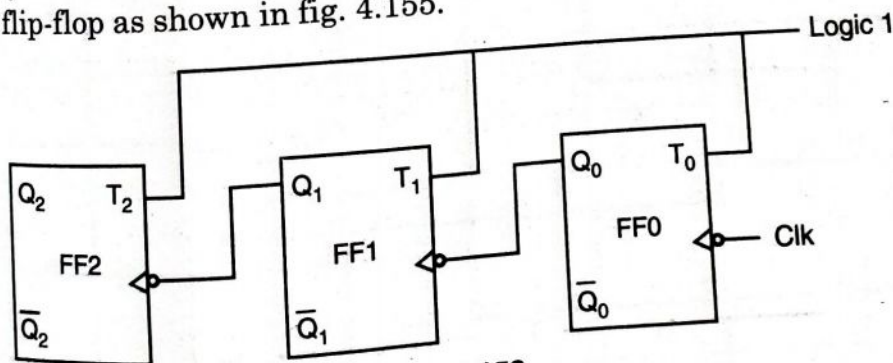


Fig. 4.152.

In this the Clk input drives FF0 and output of FF0 ( $Q_0$ ) drives FF1 and output of FF1 ( $Q_1$ ) drives FF2 which indicates a kind of asynchronous counter. T inputs i.e.,  $T_0$ ,  $T_1$ ,  $T_2$  are connected to logic 1. Here, each flip flop toggles at the negative edge of Clk pulse (as bubble is shown in clock pulse). As output of one flip flop (F/F) drives clock input of other, hence it is called as an asynchronous counter and as trigger moves like a ripple in water, hence it is



called as a ripple counter when  $Q_0$  takes a transition from 1  $\rightarrow$  0, then it can trigger FF1 means FF1 toggles and when  $Q_1$  takes a transition from 1  $\rightarrow$  0, then it can trigger FF2 means FF2 toggles. Hence overall propagation delay time is equal to sum of individual propagation delays of FF0, FF1, FF2.

$$(P.D)_{\text{Ripple counter}} = (PD)_{FF0} + (PD)_{FF1} + (PD)_{FF2}$$

### Operation:

The 3-bit ripple counter truth table is given as below

Clk	$Q_2$	$Q_1$	$Q_0$
0	0	0	0
1	0	0	1
2	0	1	0
3	0	1	1
4	1	0	0
5	1	0	1
6	1	1	0
7	1	1	1
8	0	0	0

Initially all F/Fs are cleared hence  $Q_2 = Q_1 = Q_0 = 0$ . FF0 toggles at every clock pulses on negative transition of clock. At 1st clock pulse 0  $\rightarrow$  1 transition of  $Q_0$  cannot trigger  $Q_1$  as it's a positive change hence  $Q_1 = 0$ .

Similarly 0  $\rightarrow$  0 state of  $Q_1$  cannot trigger  $Q_2$ . Hence  $Q_2 = 0$ .

In this way counter will count from 000 – 111.

### Waveform

 


Fig. 4.153.

This counter can be utilized as a frequency counter.

As time period is becoming double, hence frequency is becoming half i.e.,

$$Q_0 = \frac{1}{2} (Clk f)$$

So by using

it can count from

### PROBLEM D


(1) MoD 3

(4) MoD 7

Solution : It

$J = K = 1$  or b

(i) MoD-3

 

Divi

(ii) MoD-5





$$Q_1 = \frac{1}{4} (\text{Clk } f)$$

$$Q_2 = \frac{1}{8} (\text{Clk } f)$$

So by using three flip flops, we can get  $2^3 = 8$  distinct/unique states. Hence it can count from  $[0 - (2^3 - 1)]$  i.e., 0 - 7 states.

**PROBLEM** Design the following asynchronous (Ripple counter)

(1) MoD 3

(2) MoD 5


(3) MoD 6

(4) MoD 7

(5) MoD 9

**Solution :** It can be designed by specifically by J-K F/F counter. The condition  $J = K = 1$  or by using TF/F and  $T = 1$

(i) MoD-3

 


Divide by 3/ MOD-3 Ripple counter

MoD-3 counts f/m

	$Q_1$	$Q_0$
0 - 2 i.e.,	0	0
	0	1
	1	0
Skipped state	1	1

(ii) MoD-5

 

Divide by 5/ MoD-5 Ripple counter

MoD-5 counts f/m 0 - 4 i.e.,

$Q_2$	$Q_1$	$Q_0$
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1

Skipped states